

## F2018 MTE220 Assignment 3

userid: \_\_\_\_\_

---

Opamps are available with the following data sheet values:

$V_{OS}$	$I_B$	$I_{OS}$	$R_D$	$R_C$	$R_O$	$f_t$	$A_o$	$I_{sc}$	$L_+$	$L_-$
1 mV	1 $\mu$ A	1 nA	1 M $\Omega$	1 G $\Omega$	75 $\Omega$	1 MHz	200 k	10 mA	+ 14 V	- 14 V

where  $I_{sc}$  is the maximum current the opamp's output can supply.

---

5% PVNS (Preferred Value Numbering Systems) list: 10, 11, 12, 13, 15, 16, 18, 20, 22, 24, 27, 30, 33, 36, 39, 43, 47, 51, 56, 62, 68, 75, 82, 91.

---

A limiter circuit is required for a input signal from a 50  $\Omega$  output impedance sensor. The limiter should have a gain of  $A_v = -30.5$ , dropping to  $A_v = -205m$  when the output voltages exceeds 2.80 volts and dropping to  $A_v = -105m$  when the output voltages falls below -3.50 volts.

- Supply an input-output plot of the voltage gain function.
- Supply the circuit design using one general purpose opamp, resistors, signal diodes and a  $\pm 15$  V power supply.
- For the above circuit, what is the output voltage and opamp's output current when the input voltage is +10.0 V?
- For the above circuit, what is the output voltage and opamp's output current when the input voltage is -10.0 V?
- For the above circuit, what is the amplifier's input resistance?