

## F2018 MTE220 Assignment 7

userid: \_\_\_\_\_

Opamps are available with the following data sheet values:

$V_{OS}$	$I_B$	$I_{OS}$	$R_D$	$R_C$	$R_O$	$f_t$	$A_o$	$I_{sc}$	$L_+$	$L_-$	SR
$1\ \mu V$	$1\ \mu A$	$1\ pA$	$1\ M\Omega$	$1\ G\Omega$	$75\ \Omega$	$1\ MHz$	$200\ k$	$10\ mA$	$+14\ V$	$-14\ V$	$0.5\ V/\mu s$

where:  $I_{sc}$  is maximum current opamp can supply and SR is maximum time rate of change of opamp's output voltage

5% PVNS (Preferred Value Numbering Systems) list: 10, 11, 12, 13, 15, 16, 18, 20, 22, 24, 27, 30, 33, 36, 39, 43, 47, 51, 56, 62, 68, 75, 82, 91.

1% PVNS (Preferred Value Numbering Systems) list: 100, 102, 105, 107, 110, 113, 115, 118, 121, 124, 127, 130, 133, 137, 140, 143, 147, 150, 154, 158, 162, 165, 169, 174, 178, 182, 187, 191, 196, 200, 205, 210, 215, 221, 226, 232, 237, 243, 249, 255, 261, 267, 274, 280, 287, 294, 301, 309, 316, 324, 332, 340, 348, 357, 365, 374, 383, 392, 402, 412, 422, 432, 442, 453, 464, 475, 487, 499, 511, 523, 536, 549, 562, 576, 590, 604, 619, 634, 649, 665, 681, 698, 715, 732, 750, 768, 787, 806, 825, 845, 866, 887, 909, 931, 953, 976.

- (1) Design a single opamp inverting amplifier with a voltage gain of -100. For this amplifier, supply the small-signal input resistance, small-signal output resistance, and the small-signal -3dB bandwidth.
- (2) Design a single opamp non-inverting amplifier with a voltage gain of +100. For this amplifier, supply the small-signal input resistance, small-signal output resistance, and the small-signal -3dB bandwidth.
- (3) Design a single opamp difference amplifier with a voltage gain of 100. For this amplifier, supply the small-signal input resistances, small-signal output resistance, and the small-signal -3dB bandwidth.
- (4) Design an instrumentation amplifier with a voltage gain of 100. For this amplifier, supply the small-signal input resistances, small-signal output resistance, and the small-signal -3dB bandwidth.