

F2018 MTE220 Assignment 10

userid: _____

- (1) Supply a 3-stage MOS amplifier design with
- pmos diff amp input stage
 - nmos cascode amp second stage
 - class-AB output stage

Adjust the current mirror $\frac{W}{L}$ ratios so the first two stages are biased to the same I_D .